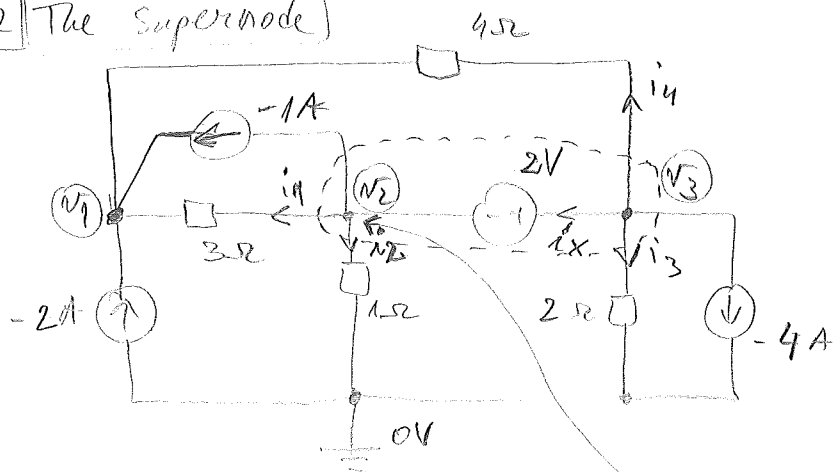


4.2 The Supernode



$v_1, v_2, v_3 = ?$

NOTE:

One way (but only now when we have one voltage source, is to select ground for nodes

(a) The hard way:

Assign a current i_x thru 2V source.

$$\text{KCL @ } v_1: \begin{cases} \frac{v_3 - v_1}{4} + \frac{v_2 - v_1}{3} + (-1) + (-2) = 0 \\ \frac{v_2 - v_1}{3} + \frac{v_2}{1} = -1 - i_x \\ \frac{v_3 - v_1}{4} + \frac{v_3}{2} + i_x + (-4) = 0 \end{cases}$$


node analysis eq's.

4 unknowns, 3 eq's

4 unknowns
4 equations!

Add also: $v_3 - v_2 = 2$

(b) Using the supernode technique

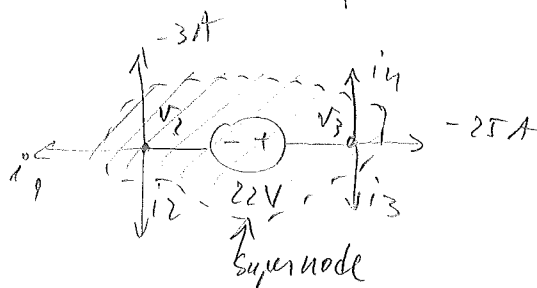

$$\begin{cases} v_1: \frac{v_3 - v_1}{4} + \frac{v_2 - v_1}{3} = \frac{12}{4} + 2 \\ v_2 + v_3: \frac{v_2 - v_1}{3} + \frac{v_2}{1} + (-1) + \frac{v_3}{2} + \frac{v_3 - v_1}{4} + (-4) = 0 \\ \text{also: } v_3 - v_2 = 2 \end{cases}$$

3 equations
3 unknowns.

(a) Using Cramer's rule:

$$\begin{vmatrix} 36 & 4 & 3 \\ 60 & 16 & 9 \\ 2 & -1 & 1 \end{vmatrix}$$

$$v_1 = \frac{\begin{vmatrix} -7 & 4 & 3 \\ -7 & 16 & 9 \\ 0 & -1 & 1 \end{vmatrix}}{\Delta}$$

$$v_2 = \frac{\begin{vmatrix} -7 & 36 & 3 \\ -7 & 20 & 9 \\ 0 & 2 & 1 \end{vmatrix}}{\Delta} = \dots$$

$$v_3 = \frac{\begin{vmatrix} -7 & 4 & 36 \\ -7 & 16 & 60 \\ 0 & -1 & 2 \end{vmatrix}}{\Delta} = \dots$$

$$\frac{36 \times 16 \times 1 + 2 \times 4 \times 9 + 3 \times 60 \times (-1) - 2 \times 3 \times 16 - 60 \times 4 \times 1 - 9 \times 36 \times (-1)}{-7 \times 16 \times 1 + 0 \times 4 \times 1 + 3 \times (-1) \times (-7) - 0 \times 16 \times 3 - 4 \times 1 \times (-7) - (-7) \times 4 \times 1} \quad [V]$$

(b) Using Gaussian elimination:

$$\left[\begin{array}{ccc|c} -7 & 4 & 3 & 36 \\ -7 & 16 & 9 & 60 \\ 0 & -1 & 1 & 2 \end{array} \right] \begin{matrix} \otimes (-1) \oplus \\ \leftarrow \end{matrix}$$

$$\left[\begin{array}{ccc|c} -7 & 4 & 3 & 36 \\ 0 & 12 & 6 & 24 \\ 0 & -1 & 1 & 2 \end{array} \right] \begin{matrix} \otimes \frac{1}{12} \oplus \\ \leftarrow \end{matrix}$$

$$\left[\begin{array}{ccc|c} -7 & 4 & 3 & 36 \\ 0 & 12 & 6 & 24 \\ 0 & 0 & \frac{5}{2} & 4 \end{array} \right]$$

$$-7v_1 + 4 \times \frac{2}{3} + 3 \times \frac{8}{3} = 36 \Rightarrow -7v_1 = 28 - \frac{8}{3}$$

$$12v_2 + 16 = 24 \Rightarrow v_2 = \frac{8}{12} \quad v = \frac{2}{3} v = v_2$$

$$\Rightarrow \boxed{v_3 = \frac{4}{\frac{5}{2}} = \frac{8}{5} \quad v}$$


$$\begin{cases} 3v_3 - 3v_1 + 4v_2 - 4v_1 = 36 \\ 4v_2 - 4v_1 + 12v_2 + 6v_3 + 3v_3 - 3v_1 = 60 \\ -v_2 + v_3 = 2 \end{cases}$$

$$\Rightarrow \begin{cases} -7v_1 + 4v_2 + 3v_3 = 36 \\ -7v_1 + 16v_2 + 9v_3 = 60 \\ -v_2 + v_3 = 2 \end{cases} \Leftrightarrow \boxed{Ax=b}$$

$$A = \begin{bmatrix} -7 & 4 & 3 \\ -7 & 16 & 9 \\ 0 & -1 & 1 \end{bmatrix} \quad X = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} \quad b = \begin{bmatrix} 36 \\ 60 \\ 2 \end{bmatrix}$$

← solved on verso of (1)

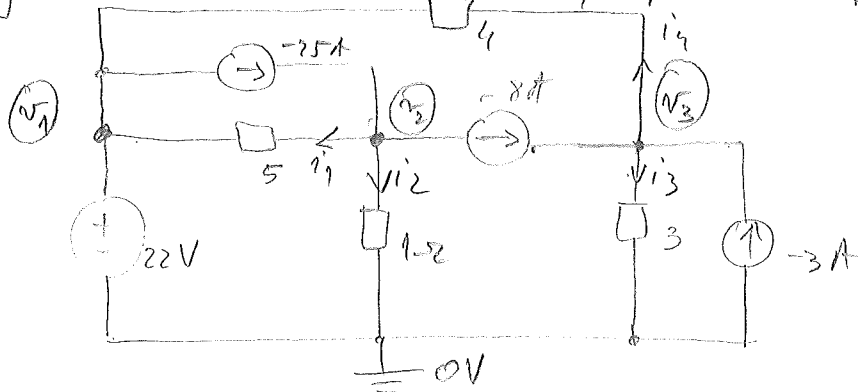© Re-selecting the reference node - not always possible and **only** if we are allowed to change reference!



Note: you could have just selected reference, w/o redrawing!

$$\begin{aligned} \text{Node } v_2: & \begin{cases} \frac{v_2 - 22}{5} + \frac{v_2}{1} - 8 = -25 \\ \Rightarrow v_2 - 22 + 5v_2 = 40 - 125 \end{cases} \\ \text{Node } v_3: & \begin{cases} \frac{v_3 - 22}{4} + \frac{v_3}{3} = -8 - 3 \\ \Rightarrow 3v_3 - 66 + 4v_3 = -11 \end{cases} \end{aligned}$$


$$\begin{cases} 6v_2 = 66 - 125 = -59 \\ 7v_3 = 55 \end{cases}$$

$$\boxed{v_2 = -\frac{59}{6} \text{ [V]}} \quad \boxed{v_3 = \frac{55}{7} \text{ [V]}}$$

Note: v_2, v_3 have values for the reference chosen!

They are not the same v_2, v_3 as in the original circuit.

Example

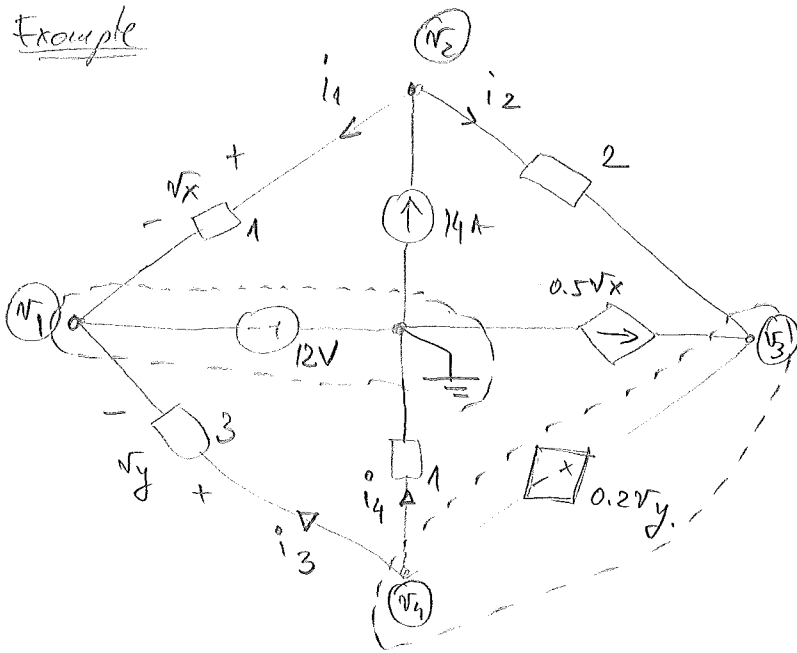

$v_1, v_2, v_3, v_4 = ?$

$v_1 = -12V$

Node v_2 :

$$14A = \frac{v_2 - (-12)}{1} + \frac{v_2 - v_3}{2}$$

Supernode v_3, v_4 :

$$0.5(v_x) + \frac{v_2 - v_3}{2} = \frac{v_4}{1} + \frac{v_4 - (-12)}{3}$$

And also:

$$v_3 - v_4 = 0.2 \times v_y = 0.2 \times (v_4 - (-12))$$

3 equations

3 unknowns: v_2, v_3, v_4 .