
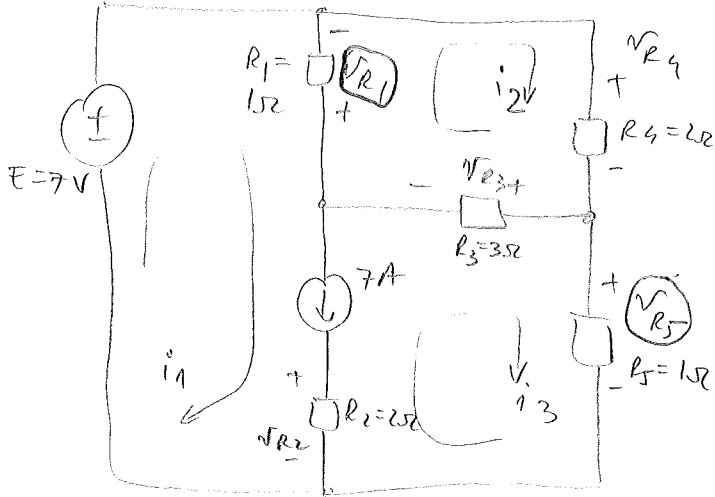


Example - from last time:

(a) one selection of voltage polarities.

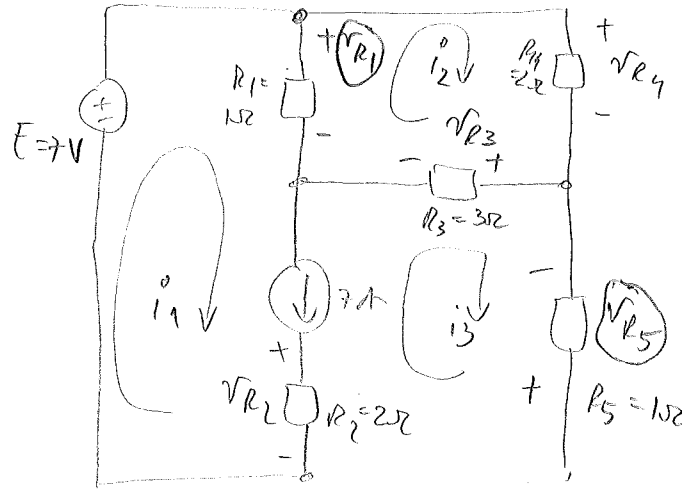

(b) another selection of voltage polarities.



loop i_2 : $\begin{cases} v_{R1} + v_{R4} + v_{R3} = 0 \\ E + v_{R1} + v_{R3} = v_{R5} \end{cases} \Rightarrow$

$\Rightarrow \begin{cases} R_1(i_2 - i_1) + R_4 i_2 + R_3(i_2 - i_3) = 0 \\ E + R_1(i_2 - i_1) + R_3(i_2 - i_3) = R_5 i_3 \end{cases}$

$\Rightarrow \begin{cases} i_2 - i_1 + 2i_2 + 3(i_2 - i_3) = 0 \\ i_2 - i_1 + 3(i_2 - i_3) - i_3 = -7 \end{cases}$

$\Rightarrow \begin{cases} -i_1 + 6i_2 - 3i_3 = 0 \\ -i_1 + 4i_2 - 4i_3 = -7 \\ i_1 - i_3 = 7 \end{cases}$

gn. of current source

$\Rightarrow \begin{cases} i_1 - 6i_2 + 3i_3 = 0 \\ i_1 - 4i_2 + 4i_3 = 7 \\ i_1 - i_3 = 7 \end{cases} \Rightarrow Ax = b$

$A = \begin{bmatrix} 1 & -6 & 3 \\ 1 & -4 & 4 \\ 1 & 0 & -1 \end{bmatrix} \quad X = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} \quad b = \begin{bmatrix} 0 \\ 7 \\ 7 \end{bmatrix}$

$i_1 = 9A \quad i_2 = 2.5A \quad i_3 = 2A$

loop i_2 : $\begin{cases} v_{R1} = v_{R4} + v_{R3} \\ E + v_{R3} = v_{R1} + v_{R5} \end{cases}$



$\Rightarrow \begin{cases} R_1(i_1 - i_2) = R_4 i_2 + R_3(i_2 - i_3) \\ E + R_3(i_2 - i_3) = R_1(i_1 - i_2) + R_5(-i_3) \end{cases}$

$\Rightarrow \begin{cases} i_1 - i_2 = 2i_2 + 3(i_2 - i_3) \\ 7 + 3(i_2 - i_3) = i_1 - i_2 - i_3 \end{cases}$


$\Rightarrow \begin{cases} -i_1 + 6i_2 - 3i_3 = 0 \\ -i_1 + 4i_2 - 4i_3 = -7 \\ i_1 - i_3 = 7 \end{cases} \quad \left. \begin{array}{l} \text{Same} \\ \text{equations!} \end{array} \right\}$

$\Rightarrow \boxed{i_1 = 9A} \quad \boxed{i_2 = 2.5A} \quad \boxed{i_3 = 2A}$


Drawing schematic diagrams

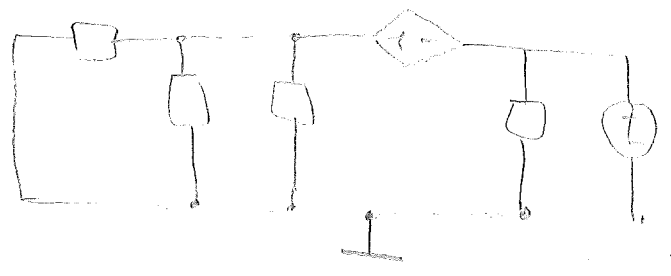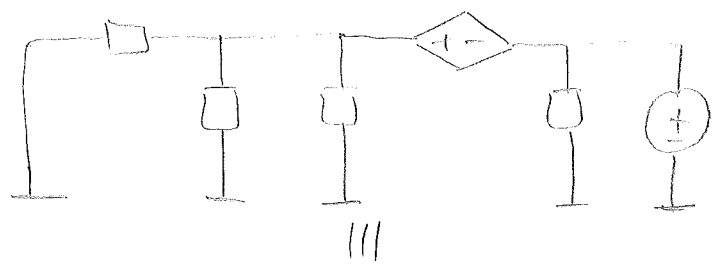

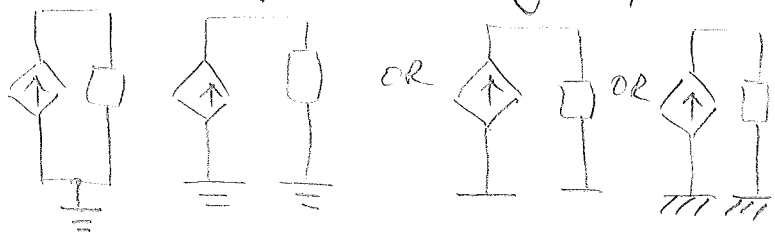You'll see articles, textbooks, etc. utilizing this drawing style:



Also, you may see:

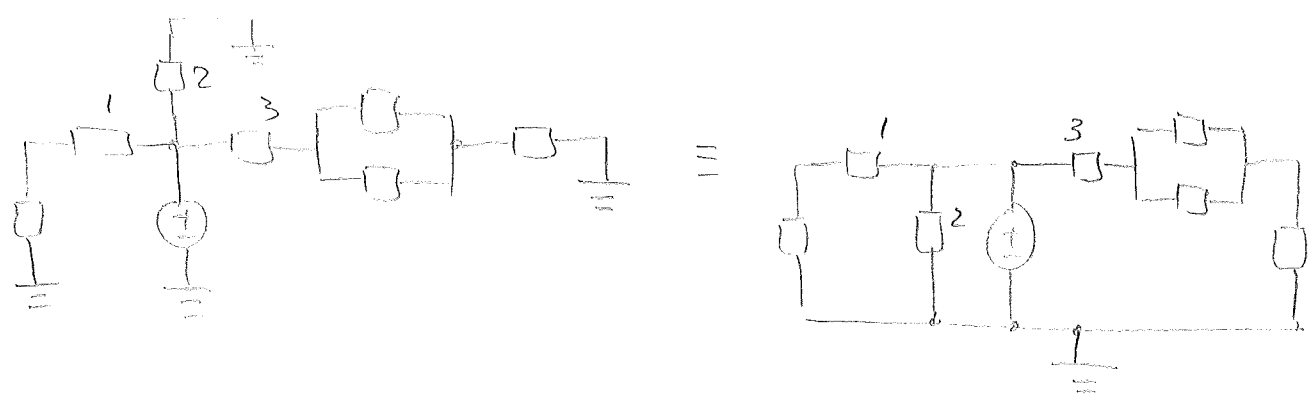

Linearity & Superposition

- We analyze linear circuits.


Def 1 - A circuit is linear if it satisfies the following properties:

(1) - the scaling property. The branch currents and node voltages resulting from a single source are linearly proportional to the source. This indicates that multiplying the source by a constant, multiplies all currents and voltages by that constant.

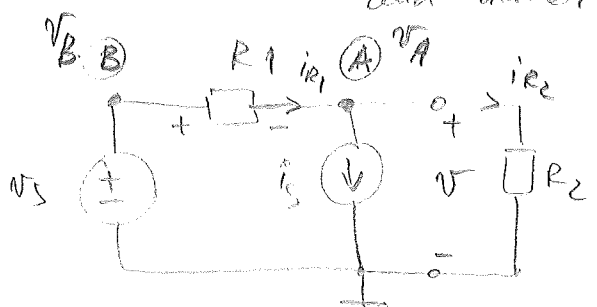
(2) - the additive property. In a circuit with multiple sources, each branch current and node voltage is the algebraic sum of the contributions from each source acting alone.

- A linear element: $v(t) = R \cdot i(t)$

Def 2 - A linear circuit: composed of independent sources, linear dependent sources, and linear elements.




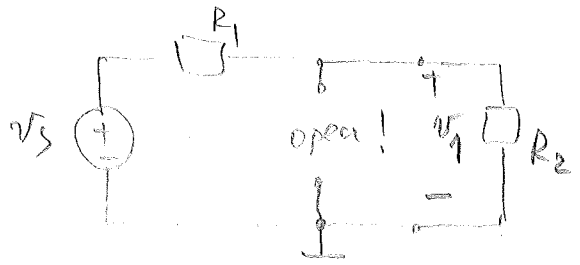(1) Contribution from v_s with $i_s = 0$. $[i_s = 0]$ is equivalent to an open circuit.




$$v_1 = \frac{R_2}{R_1 + R_2} v_s \quad \text{--- contribution of } v_s \text{ to } v.$$

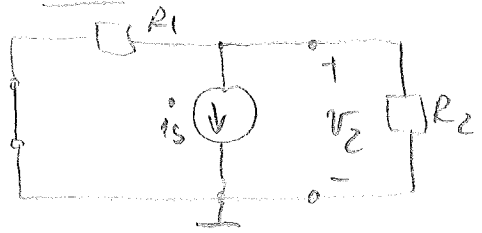(2) Contribution from i_s with $v_s = 0$. $[v_s = 0]$ represents the i-v characteristic of a short circuit:


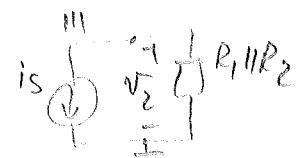
$$v_2 = -R_1 \parallel R_2 \cdot i_s = -\frac{R_1 R_2}{R_1 + R_2} i_s$$



Now, we claim that $v = v_1 + v_2$

$$v = \frac{R_2}{R_1 + R_2} v_s - \frac{R_1 R_2}{R_1 + R_2} i_s \quad (1)$$

Verification of claim by nodal analysis:

Node B: $v_B = v_s$

Node A:

$$\frac{v_B - v_A}{R_1} = i_{R_1} = \frac{v_A}{R_2} + i_s \quad \Rightarrow \quad \frac{v_s - v_A}{R_1} = \frac{v_A}{R_2} + i_s \quad \Rightarrow$$

Also: $v_A = v \quad \Rightarrow$

$$\Rightarrow R_2(v_s - v_A) = R_1 v_A + R_1 R_2 i_s$$

$$R_2 v_s - R_1 R_2 i_s = R_1 v_A + R_2 v_A$$

$$R_2 v_s - R_1 R_2 i_s = (R_1 + R_2) v_A$$

$$\Rightarrow v = v_A = \frac{R_2}{R_1 + R_2} v_s - \frac{R_1 R_2}{R_1 + R_2} i_s \quad (2)$$

← The same!

The superposition principle's essence:

Calculate the contributions from the individual independent sources alone and then superimpose these contributions algebraically!

- Useful when only a specific voltage or current is sought, since it may relieve us from solving systems of equations!
- Also useful to compare the relative contributions from various sources!