
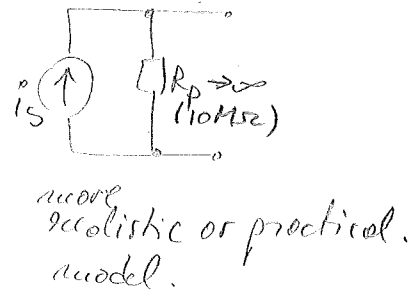
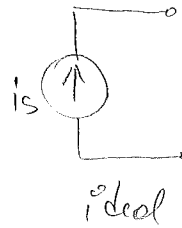
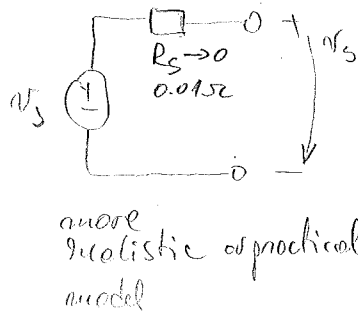



Continue w/ last page from last figure!

Source Transformations
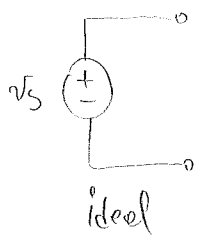
> ideal voltage and current sources do not really exist in practice!



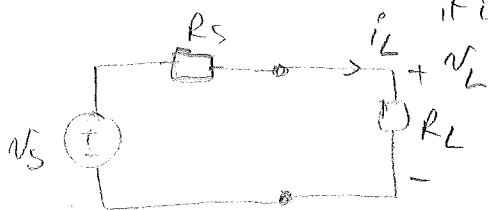$R_s \triangleq$ internal/output resistance and it is undesired!



$$(1) \quad v_L = v_s - R_s i_L$$


we would like it as large as possible such that $v_L \rightarrow v_s!$

> Open-circuit voltage: $R_L = \infty$

$$\Rightarrow i_L = \frac{v_L}{R_L} = 0 \Rightarrow v_{L_{oc}} = v_s$$

> Short-circuit current: $R_L = 0$
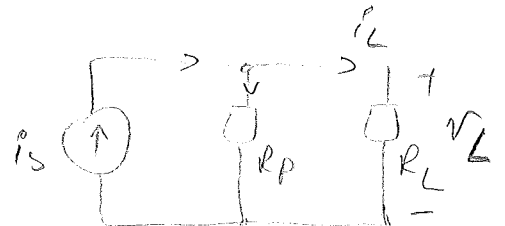
$$\Rightarrow v_L = 0 \Rightarrow i_{L_{sc}} = \frac{v_s}{R_s}$$



$$(2) \quad i_L = i_s - \frac{v_L}{R_p}$$

we would like it as large as possible such that $i_L \rightarrow i_s!$



> Open-circuit voltage: $R_L = \infty$

$$v_{L_{oc}} = R_p i_s$$

> Short-circuit current: $R_L = 0$

$$i_{L_{sc}} = i_s$$

► Equivalent practical sources

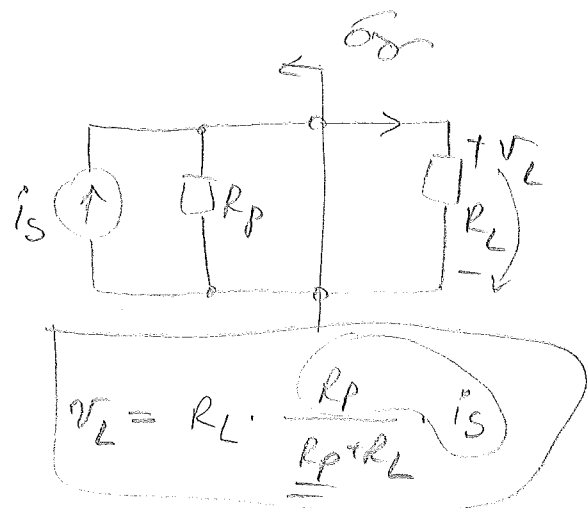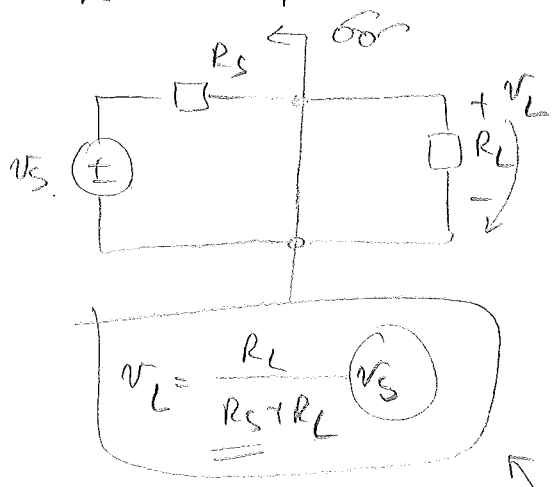


Note: could have said that i_L should be the same and get the same conclusion:

current voltage $\left\{ \begin{array}{l} V_S = R_P \cdot I_S \\ R_S = R_P \end{array} \right.$


voltage current $\left\{ \begin{array}{l} I_S = \frac{V_S}{R_P} \\ R_S = R_P \end{array} \right.$

The two practical sources are electrically equivalent (from the pov. of load R_L) if i_L and v_L are the same in both cases!!!

Example 1:

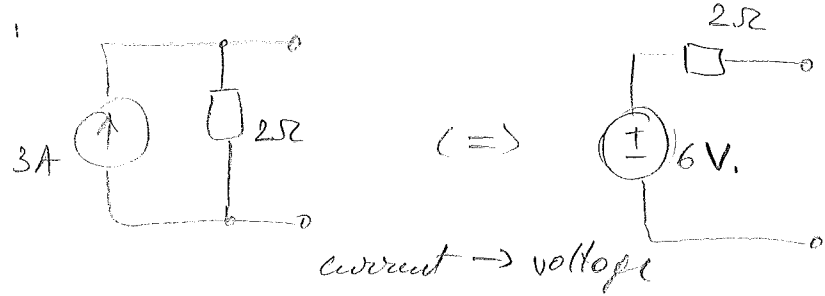

Example 2:

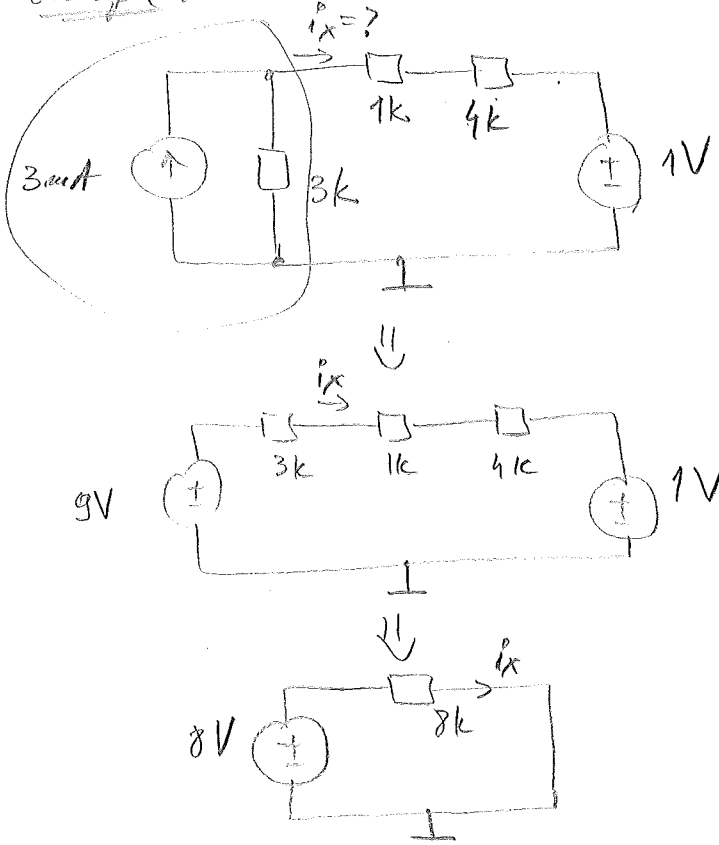


Use source transformations and simplifications!


$$i_x = \frac{8V}{8k} = 1 \mu A$$

Conclusion: The source transformation technique exploits the equivalence between a voltage source in series with a resistance AND a current source in parallel with a resistance!



voltage \rightarrow current

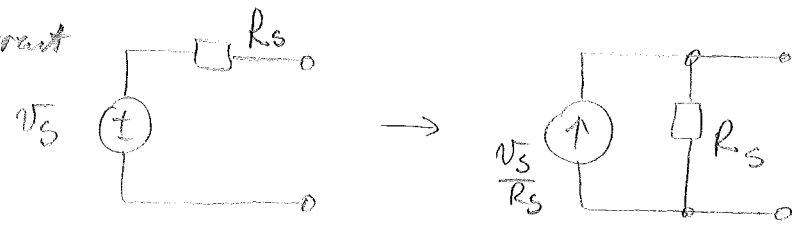




current \rightarrow voltage

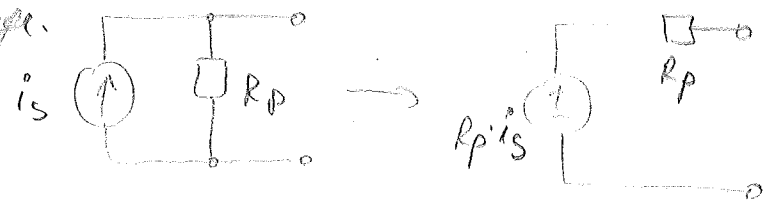

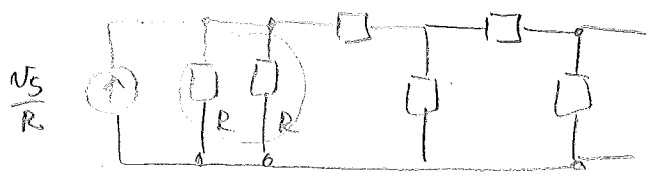
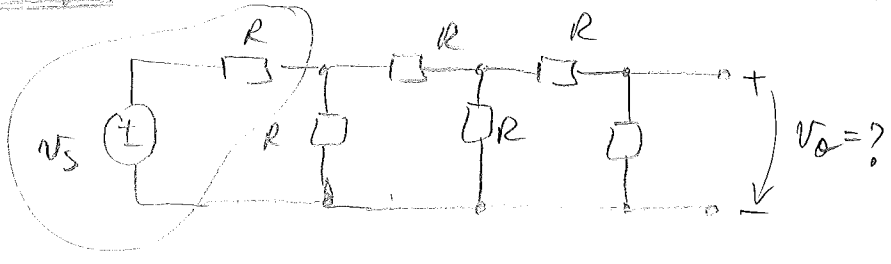
Example: Use source trans. to derive an expression for $V_o = V_o(V_S)$!



$R \parallel R = \frac{R}{2}$

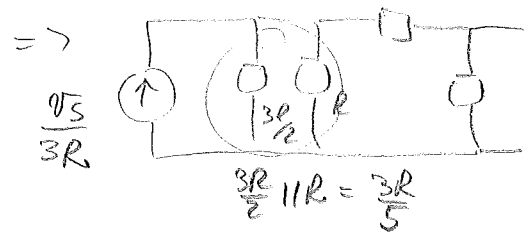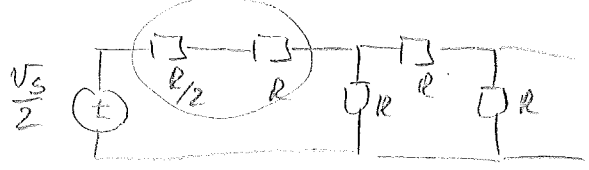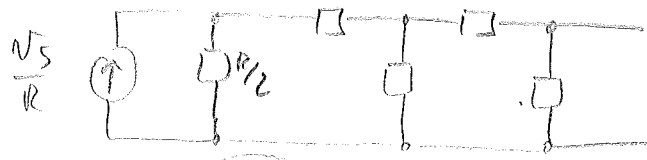

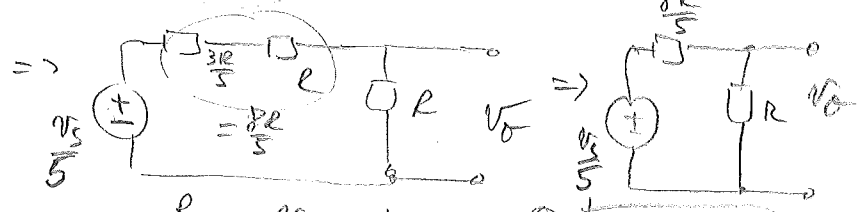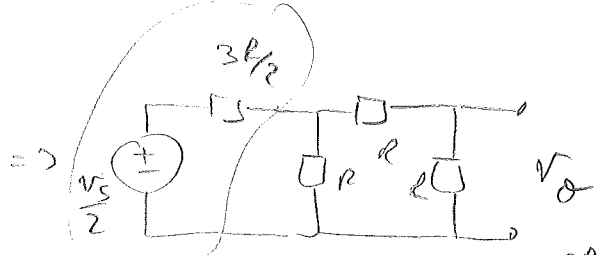$\frac{3R}{2} \parallel R = \frac{3R}{5}$



$V_o = \frac{R}{R + \frac{8R}{5}} \cdot \frac{V_S}{5} = \frac{1}{13} V_S$

$V_o = \frac{1}{13} V_S$