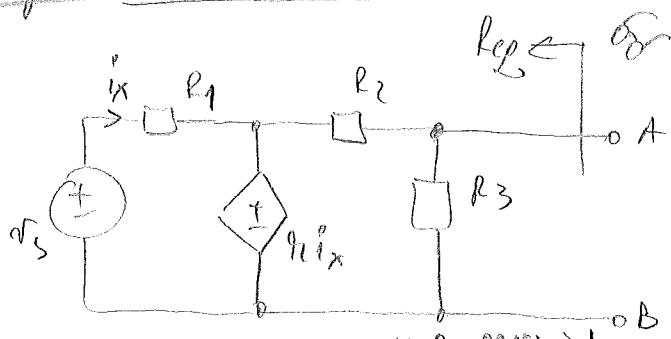



Example (Thevenin theorem)

EE-206
General way to find out R_{eq} :
work # 7
FTI (1)




$$R_{eq} = \frac{V_{oc}}{I_{sc}}$$

$$R_{eq} = \frac{V_t}{I_t}$$

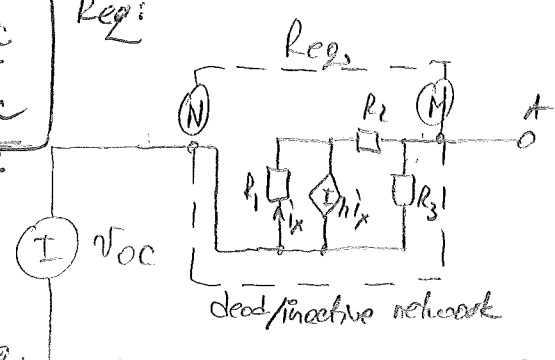

(3) R_{eq} :

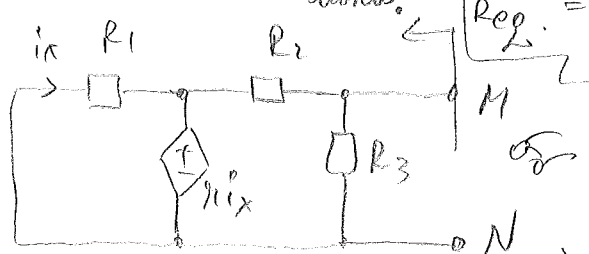


$$R_{eq} = \frac{V_{oc}}{I_{sc}}$$

Suppress ind. voltage & w/f. sources!

Do another example!

11)

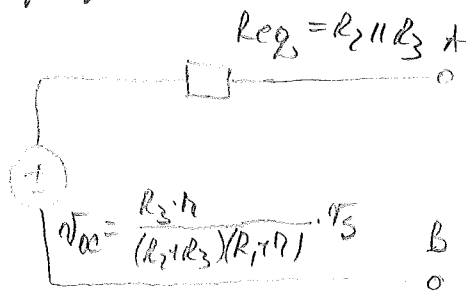


$$R_{eq} = R_2 \parallel R_3$$

$$V_{oc} = \frac{R_3 \cdot h}{(R_2 + R_3)(R_1 + h)} \cdot v_s$$

From eq. (1) & (2) $R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{R_3 \cdot h}{(R_2 + R_3)(R_1 + h)} \cdot v_s}{\frac{h}{R_2} \cdot \frac{v_s}{R_1 + h}} = \frac{R_2 R_3}{R_2 + R_3} = R_2 \parallel R_3$

$$R_{eq} = R_2 \parallel R_3 \quad (3)$$

(1) V_{oc}

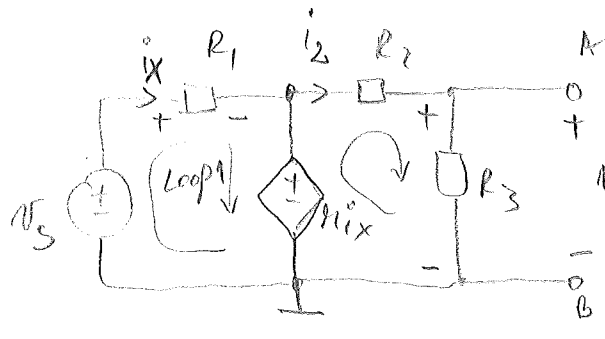


$$V_{oc} = \frac{R_3}{R_2 + R_3} \cdot h i_x$$

voltage division.

KVL Loop 1: $v_s = R_1 i_x + h i_x \Rightarrow i_x = \frac{1}{R_1 + h} \cdot v_s$

$$\Rightarrow V_{oc} = \frac{R_3 \cdot h}{(R_2 + R_3)(R_1 + h)} \cdot v_s \quad (1)$$

(2) I_{sc}

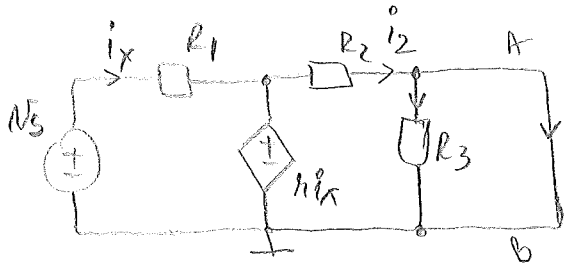

$$I_{sc} = i_2 = \frac{h i_x}{R_2} = \frac{h}{R_2} \cdot \frac{1}{R_1 + h} \cdot v_s = I_{sc} \quad (2)$$