


Circuit theorems: Thévenin and Norton equivalent circuits.

Definitions:

One-port = a network with just one pair of terminals emerging from it is called a one-port network, or a one-port for short.

i-v characteristic:

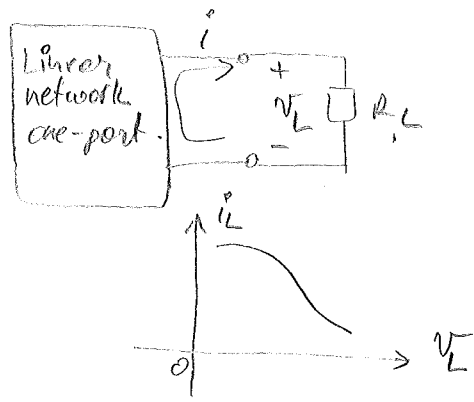- open-circuit voltage V_{oc}
- short-circuit current I_{sc}




- equivalent resistance of the one-port: R_{eq}

with all voltage and current sources in the network suppressed!

It is given by:

$$R_{eq} = \frac{V_{oc}}{I_{sc}}$$


(see last page for proof).

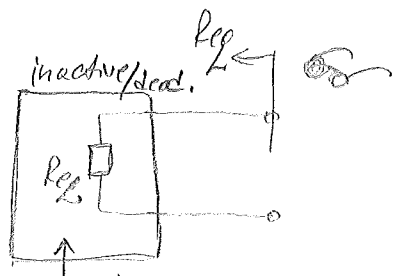


- The most general technique $R_{eq} = \frac{V_{test}}{I_{test}}$ because I_{sc} or V_{oc} may be zero! in pathological examples

Thévenin's theorem

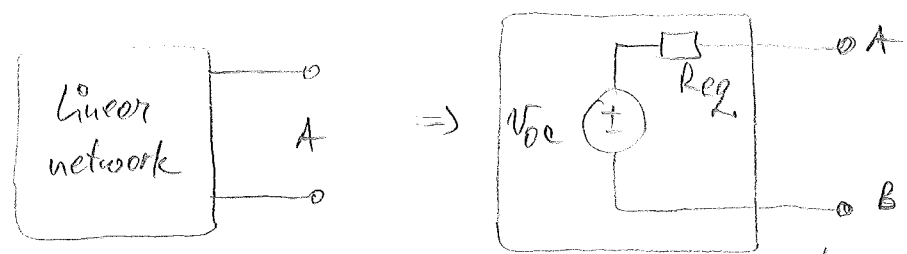
Any linear resistive one-port is equivalent to an ideal voltage source V_{oc} in series with a resistance R_{eq} , where V_{oc} and R_{eq} are: the open-circuit voltage and the equivalent resistance of the one-port!



If the linear network has dependent sources and the controlling variables are within the network, then R_{eq} is the network as seen at terminals A, B with sources suppressed! (i.e. the dead/inactive network) Only the independent ones!

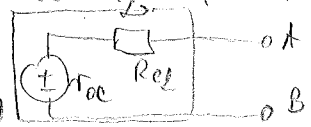


Example 1:

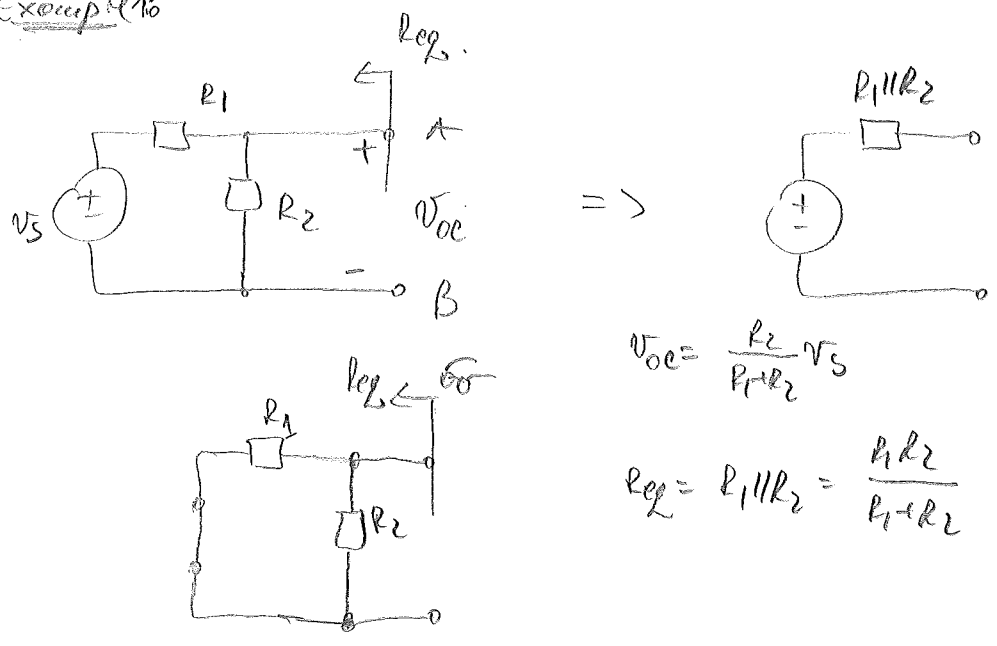

$$V_{oc} = \frac{R_2}{R_1 + R_2} V_S$$


$$R_{eq} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Example 2: (skip)

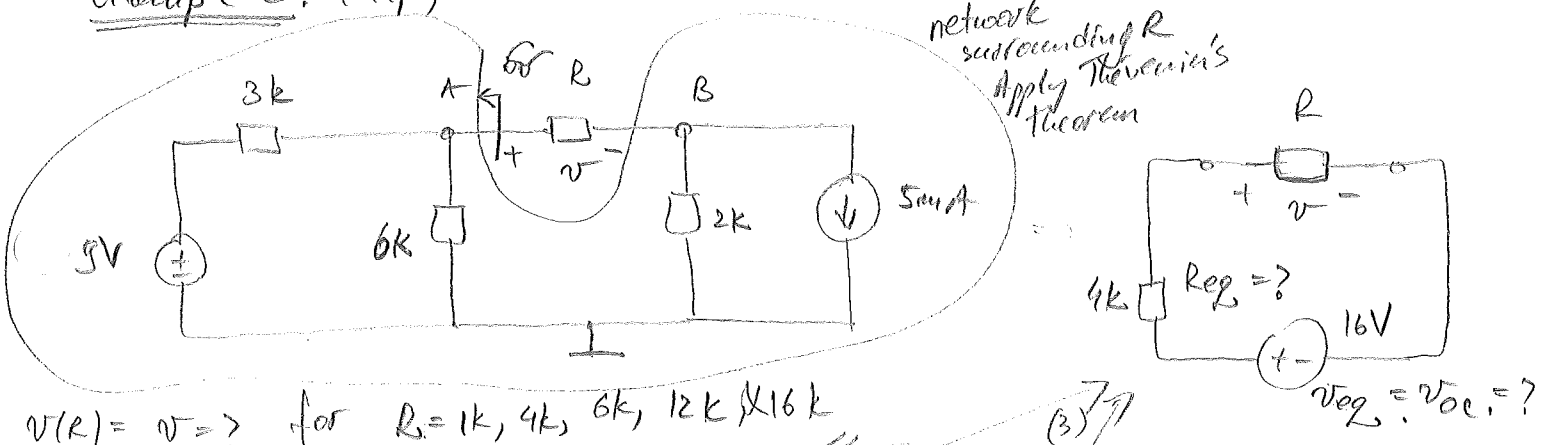

$V(R) = v \Rightarrow$ for $R = 1k, 4k, 6k, 12k, 16k$

Method 1:

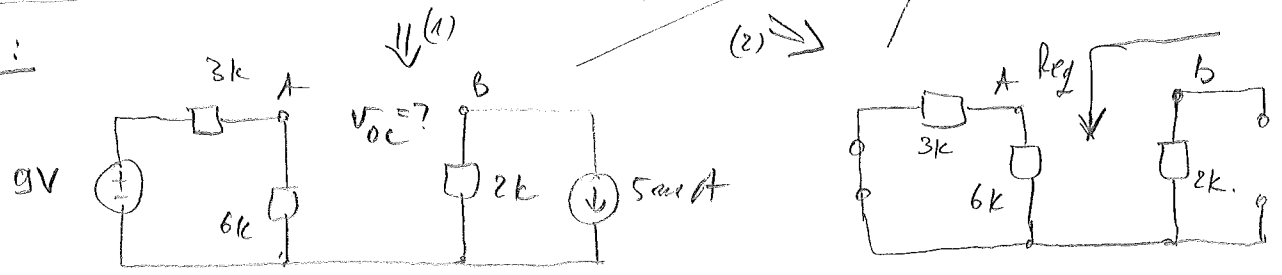

$$V_{oc} = v_A - v_B = \frac{6k \times 9V}{(3+6)k} - (2k \times 5mA) = (6+10)V = 16V$$

$$R_{eq} = 2k + (3 || 6)k = (2 + \frac{3 \cdot 6}{3+6})k = 4k$$


$$v = \frac{R}{R_{eq} + R} \cdot V_{oc} = \frac{R}{R + 4k} \cdot 16V = v(R)$$

- $R = 1k \Rightarrow v = \frac{16}{5} V$
- $R = 4k \Rightarrow v = 8V$
- $R = 6k \dots$

Method 2: Use nodal analysis.





Norton's Theorem

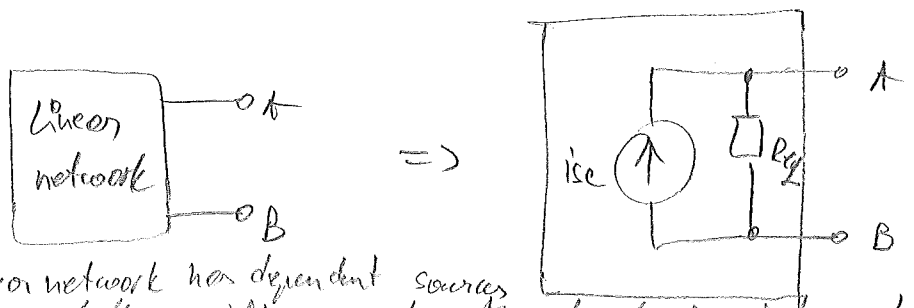- Any linear resistive one-port is equivalent to an ideal current source i_{sc} in parallel with a resistance R_{eq} , where i_{sc} and R_{eq} are the short-circuit current and the equivalent resistance of the one-port network.





if the linear network has dependent sources and the controlling variables are within the network R_{eq} is the dead/inactive network!



Example 1:

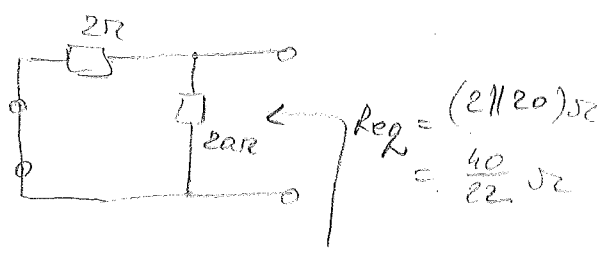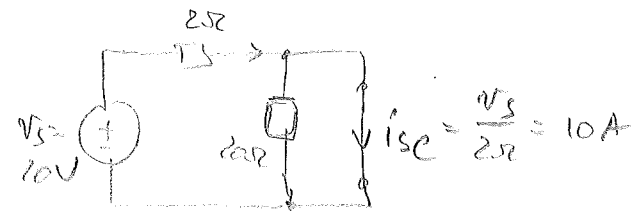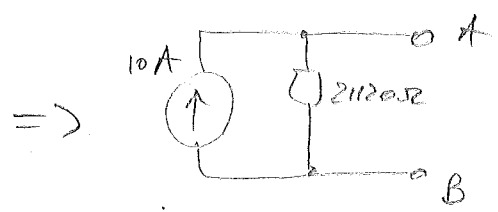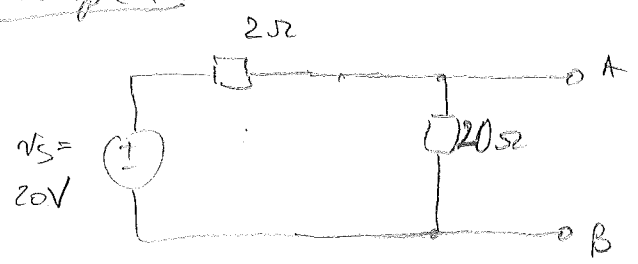

Example 2:

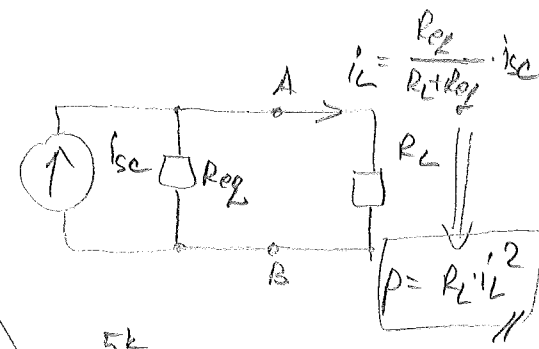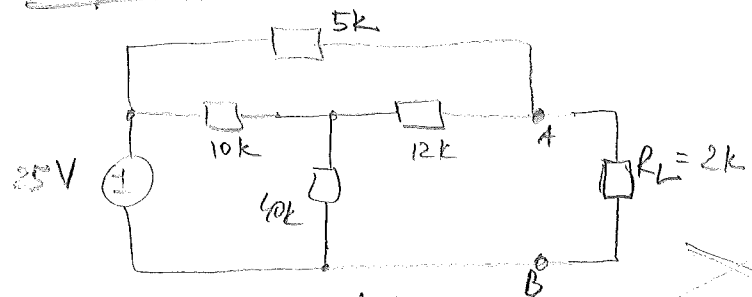

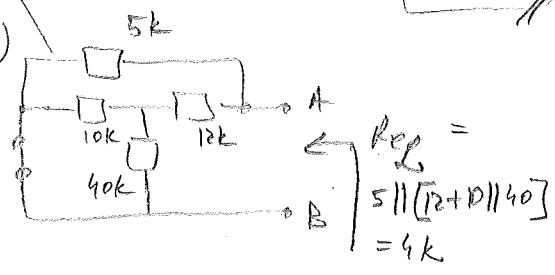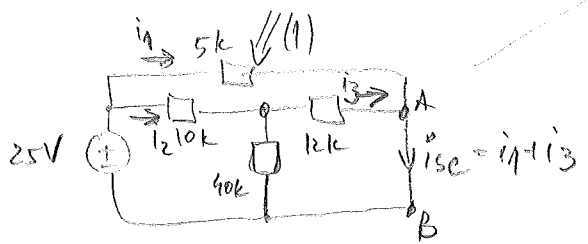Use Norton's equivalent to find the power in R_L !



$i_1 = \frac{25V}{5k} = 5mA$


$i_3 = \frac{1}{2} \times \frac{40}{40 || 12} = \frac{40}{52} i_2$; $i_2 = \frac{25V}{10 + 40 || 12} = 1.3mA$

$\Rightarrow i_{sc} = 5mA + 1.3mA = 6.3mA$

Extra material
Proof of $R_{eq} = \frac{V_{oc}}{I_{sc}}$

OBS: not covered in class normally \rightarrow no time.


Method 1: i-v characteristics

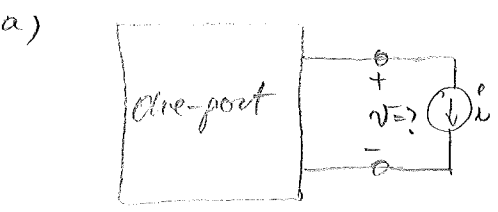


contribution of port
contribution of i

$$v = v_1 + v_2$$

Use superposition:

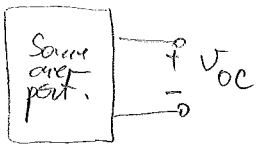


$$v_1 = v_{oc}$$

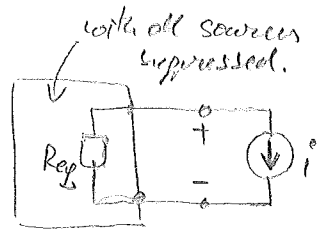


$$v_2 = -R_{eq} \cdot i$$
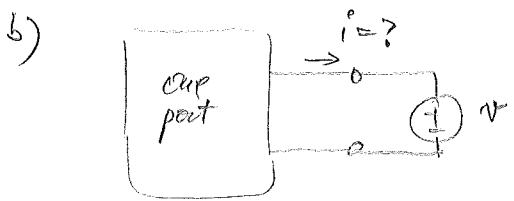
$$\Rightarrow v = v_{oc} - R_{eq} \cdot i \quad (1)$$




$$i = i_1 + i_2$$

Use superposition:

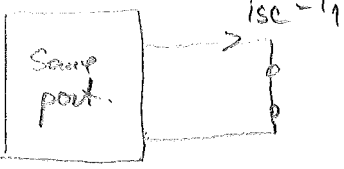

$$i_1 = i_{sc}$$

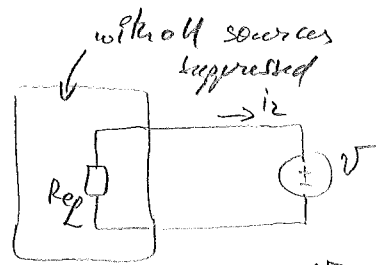

$$i_2 = -\frac{v}{R_{eq}}$$

$$\Rightarrow i = i_{sc} - \frac{v}{R_{eq}} \quad (2)$$


They are equivalent if i-v characteristics are the same!

$$\frac{V_{oc}}{R_{eq}} = I_{sc} \Rightarrow R_{eq} = \frac{V_{oc}}{I_{sc}} \quad \underline{\underline{nice!}}$$

Method 2 of finding $R_{eq} = ?$

- Steps: (1) suppress all v, i sources of the one-port network
(2) apply a test voltage v_t and measure/ find current i_t .

$$(3) R_{eq} = \frac{v_t}{i_t}$$

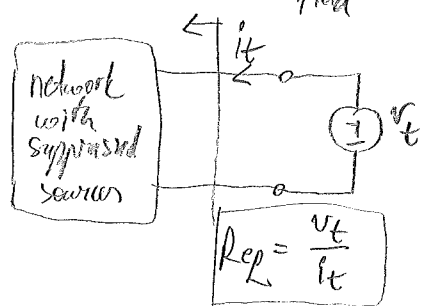

or apply i_t and find v_t !