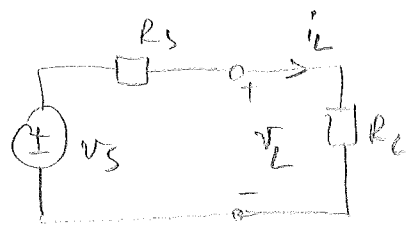


## Maximum power transfer theorem



practical  
voltage  
source

Power delivered to the load  $R_L$ :

$$P_L = i_L^2 \cdot R_L = \frac{v_s^2 \cdot R_L}{(R_L + R_s)^2} \quad (1)$$

$$i_L = \frac{v_s}{R_s + R_L}$$

Differentiate w.r.t  $R_L$  to find the maximum value of  $R_L$  that absorbs maximum power from the practical voltage source.

$$(1) \Rightarrow \frac{dP_L}{dR_L} = \frac{(R_L + R_s)^2 \cdot v_s^2 - v_s^2 \cdot R_L \cdot 2 \cdot (R_L + R_s)}{(R_L + R_s)^4}$$

$$\frac{dP_L}{dR_L} = 0 \Rightarrow (R_L + R_s)^2 \cdot v_s^2 - v_s^2 \cdot R_L \cdot 2(R_L + R_s) = 0$$

$$R_L + R_s - 2R_L = 0 \Rightarrow \boxed{R_L = R_s} \quad (2)$$


(i) Theorem: an independent voltage source in series with a resistance  $R_s$  (or an independent current source in parallel with a resistance  $R_s$ ) delivers a maximum power to that load resistance  $R_L$  for which  $R_L = R_s$ !

(ii) A network delivers the maximum power to a load resistance  $R_L$  when (load-part)  $R_L$  is equal to the Thevenin equivalent resistance of the one-port network!


what is that power?

$$P_{L, \max} = \frac{v_s^2 \cdot R_s}{(R_s + R_s)^2} = \left[ \frac{v_s^2}{4R_s} = P_{L, \max} \right] \quad (3)$$

Example:

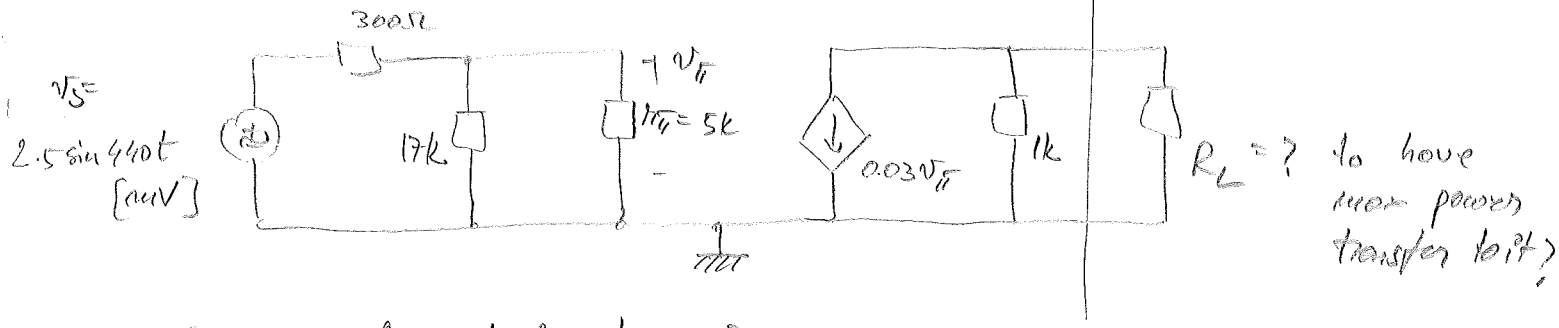

Thevenin's equivalent resistance?

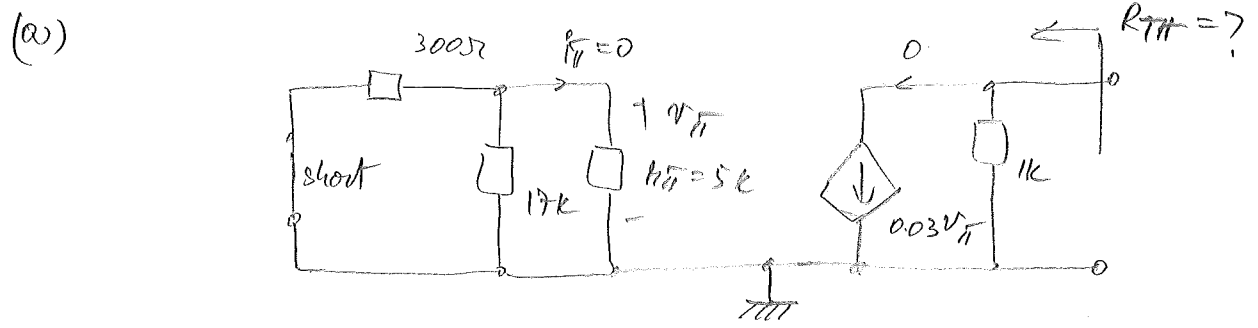


Method 1:

$$i_{\pi} = 0 \Rightarrow v_{\pi} = 0 \Rightarrow 0.03 v_{\pi} = 0 \Rightarrow R_{TH} = 1k$$

Method 2:  $R_{eq} = \frac{v_{oc}}{i_{sc}}$

$\Rightarrow$  To get maximum power we need  $R_L = R_{TH} = 1k$ !

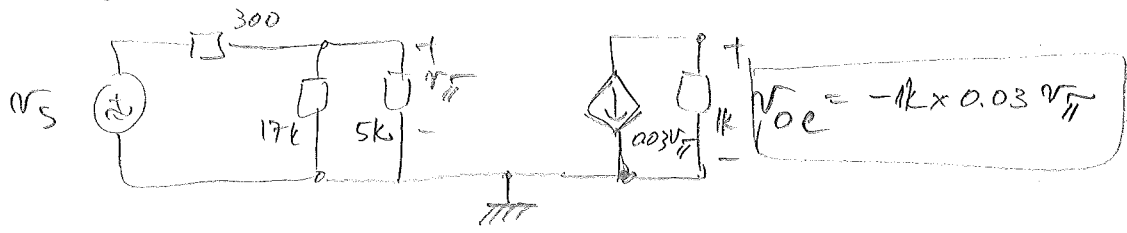Find  $v_{oc}$  (anyway needed for the Thevenin's equivalent)



$$v_{\pi} = \frac{5117}{5117 + 300} v_s \Rightarrow v_{oc} = -0.03k \cdot v_{\pi} = -0.03k \times \frac{5117}{5117 + 300} v_s = -0.03k \times \frac{5117}{5417} v_s = -0.03k \times 0.944 v_s = -0.02832k v_s$$



$$\Rightarrow R_{TH} = \frac{v_{oc}}{i_{sc}} = \frac{-1k \times 0.03 v_{\pi}}{-0.03 v_{\pi}} = 1k = R_{TH}$$

(b) Max power value?



We need  $v_{oc} = v_{TH} = ?$

$$v_{oc} = -0.03k \times \frac{3864}{3864 + 300} v_s = -68.6 \sin 440t \text{ [mV]}$$



$$\Rightarrow P_{max} = \frac{v_{TH}^2}{4R_{TH}} = 1.211 \sin^2 440t \text{ [uW]}$$

Delta-Wye conversion

$\Delta \rightarrow Y$  ← Homework!

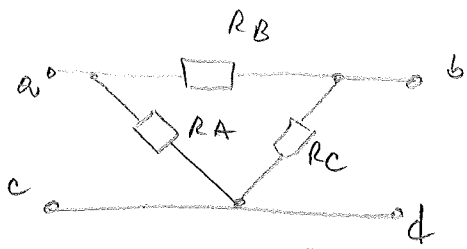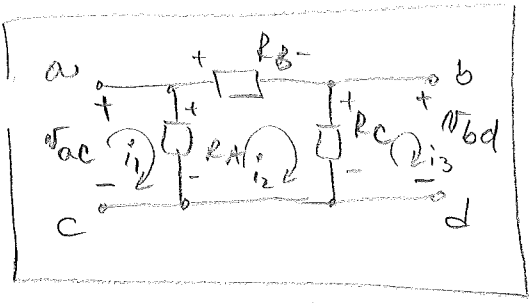

how? ↓ (?)

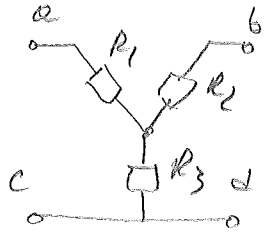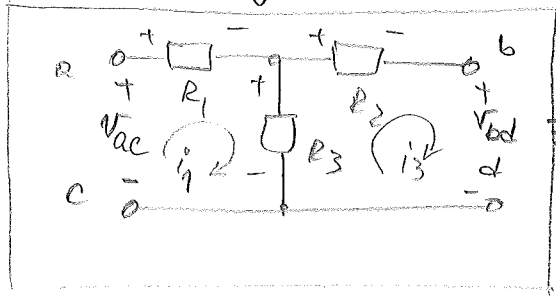

Networks are equivalent if terminal voltages and currents are equal!

Method 1: Do mesh analysis:

$$\begin{cases} v_{ac} = R_A(i_1 - i_2) \\ R_A(i_1 - i_2) = R_B i_2 + R_C(i_2 - i_3) \\ R_C(i_2 - i_3) = v_{bd} \end{cases}$$

$$\begin{cases} v_{ac} = R_1 i_1 + R_3(i_1 - i_3) = (R_1 + R_3)i_1 - R_3 i_3 \\ R_3(i_1 - i_3) + R_2 i_3 = v_{bd} = -R_2 i_1 + (R_2 + R_3)i_3 \end{cases}$$

remove  $i_2$

$$\rightarrow v_{ac} = \left( R_A - \frac{R_A^2}{R_A + R_B + R_C} \right) i_1 - \frac{R_A R_C}{R_A + R_B + R_C} i_3$$

$$\rightarrow v_{db} = -\frac{R_A R_C}{R_A + R_B + R_C} i_1 + \left( R_C - \frac{R_C^2}{R_A + R_B + R_C} \right) i_3$$

compare =


(2)  $\Rightarrow$   $\Delta \rightarrow Y$

$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C} \quad R_2 = \frac{R_A R_C}{R_A + R_B + R_C} \quad R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$



(3)  $\Rightarrow$   $Y \rightarrow \Delta$

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} \quad R_B = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} \quad R_C = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

see versal 2

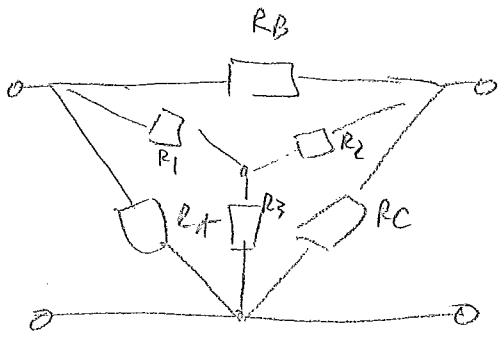

Method 2:

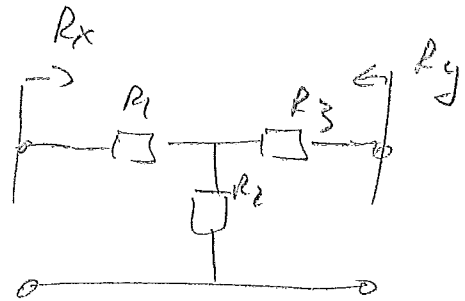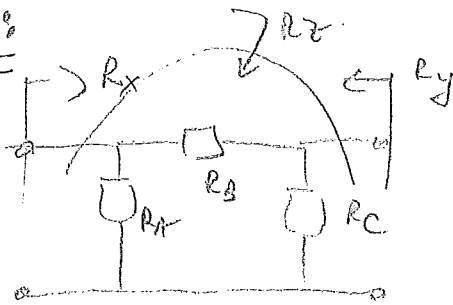

$$R_x = R_A \parallel (R_B + R_C) = \frac{R_A (R_B + R_C)}{R_A + R_B + R_C}$$

$$R_y = R_C \parallel (R_B + R_A) = \frac{R_C (R_B + R_A)}{R_A + R_B + R_C}$$


$$R_z = R_B \parallel (R_A + R_C) = \frac{R_B (R_A + R_C)}{R_A + R_B + R_C}$$

$$R_x = R_1 + R_2$$

$$R_y = R_2 + R_3$$

$$R_z = R_1 + R_3$$


=>

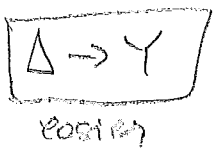

$$\Rightarrow R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$
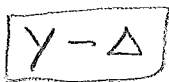
$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$



more difficult

$$\Rightarrow R_A =$$

$$R_B =$$

$$R_C =$$