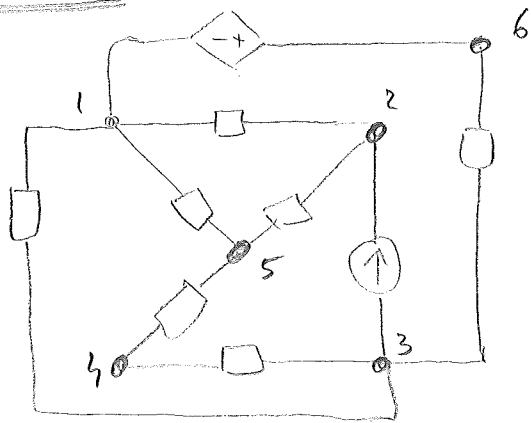



Trees and general nodal analysis

Definitions:



circuit:





=>

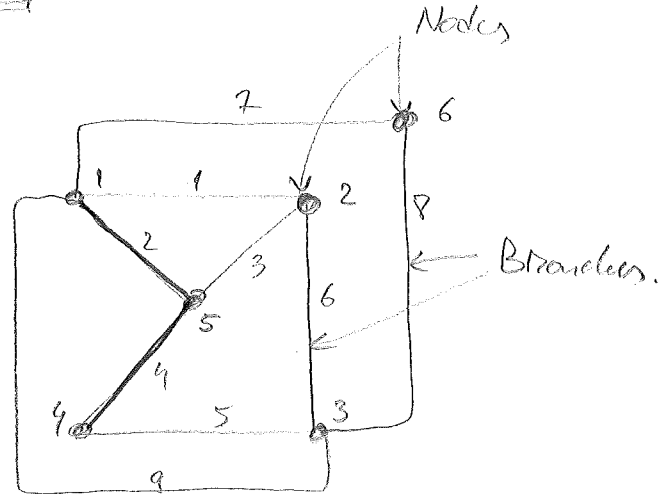

(Linear) graph = (Nodes, Branches) =  $G(V, E)$   
 corresponding to (vertices), (edges)  $N=6$   
 the circuit. (Edges)  $|E|=9$

Path from 1 to 4: {1, 5, 4}  
 Another path from 1 to 4: {1, 6, 3, 4}  
Loop = closed path.

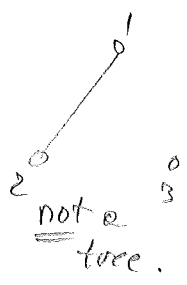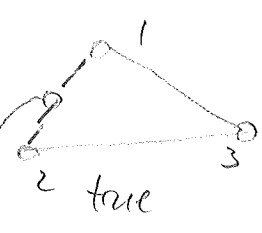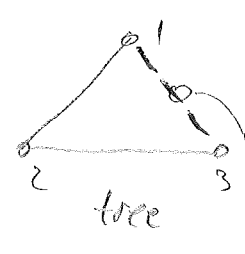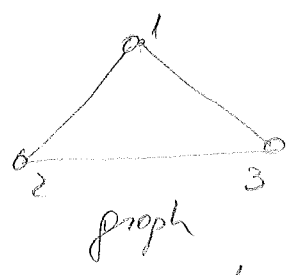
Tree = a set of branches that connect all nodes with no loop!



How many trees are there?

Cotree = the complementary set of edges of a tree.

cotrees

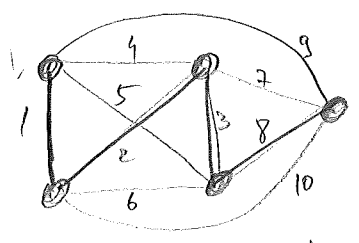

red is the tree = {1, 2, 3, 8}  
 cotree = {4, 5, 6, 7, 9, 10}

link is a branch  $\in$  cotree.

Cracks!

General

Method to write a set of nodal equations

0 - Given circuit

1 - Draw graph, identify a tree

2 - Place all voltage sources in the tree (dependent & independent)

3 - Place all current sources in the cotree (-|| & ||)



4 - Place all control voltage branches for voltage-controlled dependent sources in the tree, if possible.

5 - Place all control current -||- in current-controlled -||- in the cotree, if possible.

6 - Assign voltage variables.

7 - Write a set of equations using KCL for all but one nodes and supernodes!

Example:

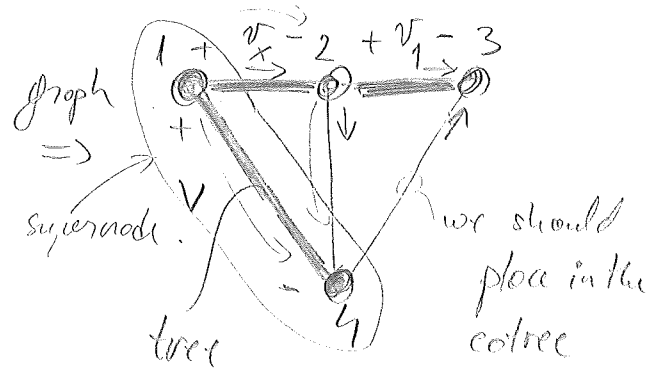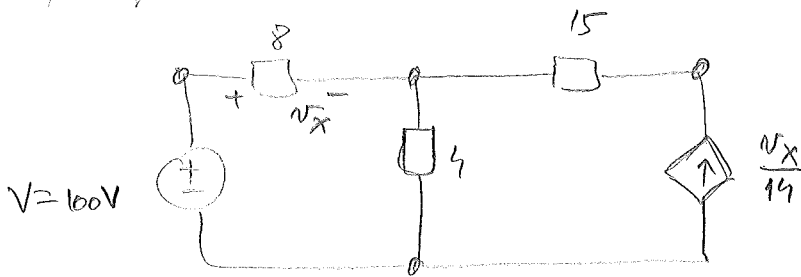

KCL Node 3:  $\frac{v_1}{15} + \frac{v_x}{14} = 0$

KCL Node 2:  $\frac{v_x}{8} = \frac{v_1}{15} + \frac{v - v_x}{4}$  found along the path between nodes 2 & 4 in the tree!

The only 2 unknowns are  $v_x$  and  $v_1$ .

$$\begin{cases} \frac{v_1}{15} + \frac{v_x}{14} = 0 \\ \frac{4v_1}{15} + \frac{3v_x}{4} = \frac{1500}{4} \end{cases} \Rightarrow \begin{cases} 14v_1 + 15v_x = 0 \\ -4v_1 + 45v_x = 1500 \end{cases} \Rightarrow \begin{cases} Ax = b \\ v_1 = 60 \text{ V} \\ v_x = 56 \text{ V} \end{cases}$$

$$A = \begin{bmatrix} 14 & 15 \\ -4 & 45 \end{bmatrix} \quad b = \begin{bmatrix} 0 \\ 1500 \end{bmatrix} \quad x = \begin{bmatrix} v_1 \\ v_x \end{bmatrix}$$