
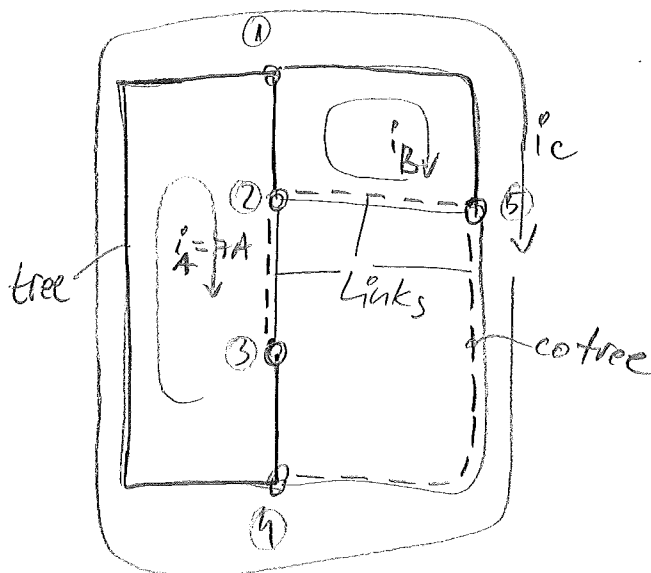


Links and general loop analysis

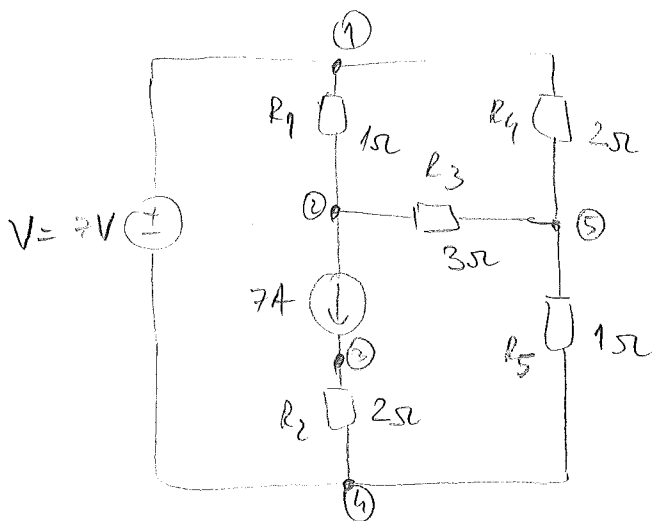- The dual of the method of writing nodal equations.
- Similar steps as in the other method (the general nodal analysis)
- However now we assign current to each element in the cotree



> assign currents to branches in the cotree

> see these currents as loop currents thru loops constructed using the link & the tree cotree-branch.

Write KVL equations around these loops:

first: $i_A = 7A$

$$\left. \begin{aligned} i_B \text{ loop: } R_1(i_B - i_A) + R_4(i_B + i_C) + R_3(i_B) &= 0 \\ i_C \text{ loop: } -7V + R_4(i_B + i_C) + R_5 i_C &= 0 \end{aligned} \right\} \Rightarrow \begin{cases} (i_B) - 7 + 2i_B + 2i_C + 3i_B = 0 \\ -7 + 2i_B + 2i_C + i_C = 0 \end{cases}$$


$$\Rightarrow \begin{cases} 6i_B + 2i_C = 7 \\ 2i_B + 3i_C = +7 \end{cases} \quad A = \begin{bmatrix} 6 & 2 \\ 2 & 3 \end{bmatrix} \quad b = \begin{bmatrix} 7 \\ -7 \end{bmatrix} \quad x = \begin{bmatrix} i_B \\ i_C \end{bmatrix} \Rightarrow$$

$$\Rightarrow \boxed{AX = b}$$


$$i_B = \frac{\begin{vmatrix} 7 & 2 \\ -7 & 3 \end{vmatrix}}{\begin{vmatrix} 6 & 2 \\ 2 & 3 \end{vmatrix}} = \frac{21 - 14}{18 - 4} = \frac{7}{14} = \frac{1}{2} = \boxed{0.5 A = i_B} \quad \boxed{i_A = 7 A}$$

$$i_C = \frac{\begin{vmatrix} 6 & 7 \\ 2 & -7 \end{vmatrix}}{\begin{vmatrix} 6 & 2 \\ 2 & 3 \end{vmatrix}} = \frac{42 - 14}{14} = \frac{28}{14} = \boxed{2 A = i_C}$$

Example

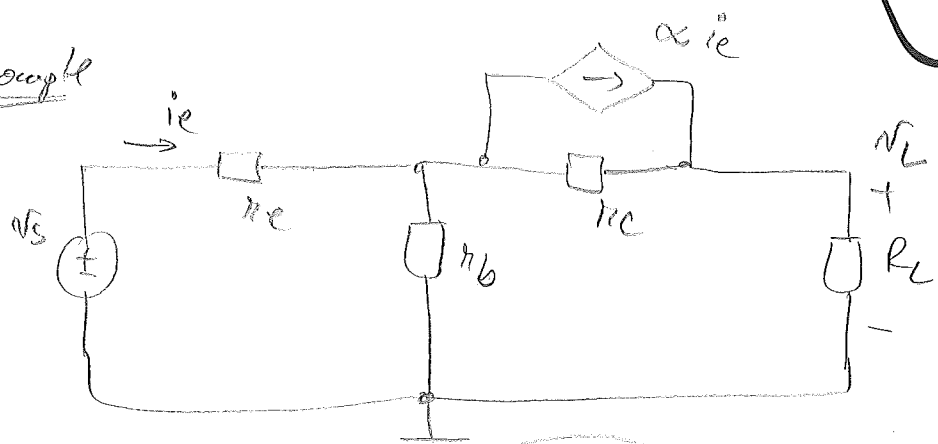

$i_e = ?$
 $v_L = ?$

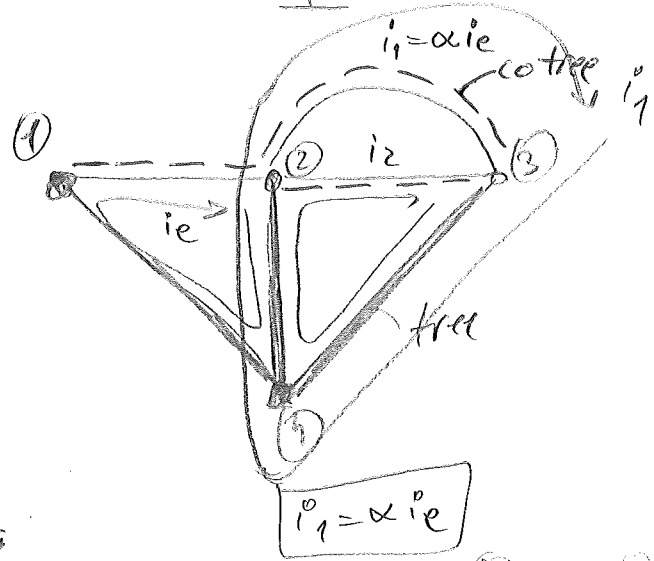

$G(V, E)$
N nodes B branches

Loop i_e : $-v_s + r_e(i_e) + r_b(i_e - i_2 - \alpha i_e) = 0$
 Loop i_2 : $r_b(i_2 + \alpha i_e - i_e) + r_c(i_2) + r_L(i_2 + \alpha i_e) = 0$

$\Rightarrow \begin{cases} [r_e + (1-\alpha)r_b]i_e - r_b i_2 = v_s \\ [r_b(\alpha-1) + \alpha r_L]i_e + (r_b + r_c + r_L)i_2 = 0 \end{cases}$

$A = \begin{bmatrix} r_e + (1-\alpha)r_b & -r_b \\ \alpha r_L - (1-\alpha)r_b & r_b + r_c + r_L \end{bmatrix} \quad b = \begin{bmatrix} v_s \\ 0 \end{bmatrix} \quad x = \begin{bmatrix} i_e \\ i_2 \end{bmatrix}$

$i_e = \frac{\begin{vmatrix} v_s & -r_b \\ 0 & r_b + r_c + r_L \end{vmatrix}}{\begin{vmatrix} r_e + (1-\alpha)r_b & -r_b \\ \alpha r_L - (1-\alpha)r_b & r_b + r_c + r_L \end{vmatrix}} = \frac{r_b + r_c + r_L}{() () + r_b ()} \cdot v_s$


$i_2 = \frac{\begin{vmatrix} r_e + (1-\alpha)r_b & v_s \\ \alpha r_L - (1-\alpha)r_b & 0 \end{vmatrix}}{\begin{vmatrix} r_e + (1-\alpha)r_b & -r_b \\ \alpha r_L - (1-\alpha)r_b & r_b + r_c + r_L \end{vmatrix}} = -\frac{\alpha r_L - (1-\alpha)r_b}{() () + r_b ()} \cdot v_s$

$v_L = r_L(i_1 + i_2)$

M1

Repeat nodal analysis

①

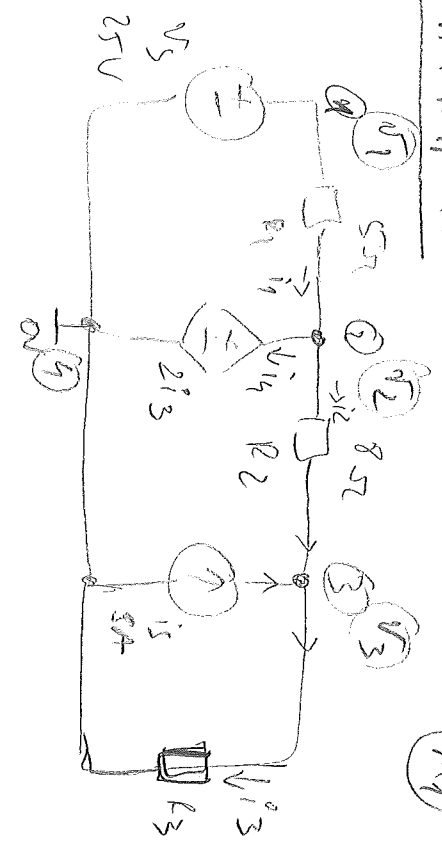

$$\begin{cases} v_1 = v_5 \\ v_2 = 2i_3 \\ v_3 = ? = i_3 R_3 \end{cases}$$


we know,

2 unknown only.

$$\begin{aligned} \textcircled{2} \quad v_1 - v_2 + \frac{v_2 - v_3}{R_2} &= i_4 \\ \textcircled{3} \quad \frac{v_1 - v_3}{R_2} + i_5 &= \frac{v_3}{R_3} \end{aligned}$$

$$\begin{cases} \frac{v_1 - 2i_3}{R_1} + \frac{2i_3 - i_3 R_3}{R_2} = i_4 \\ \frac{2i_3 - i_3 R_3}{R_2} + i_5 = i_3 \end{cases}$$

M2 General nodal analysis

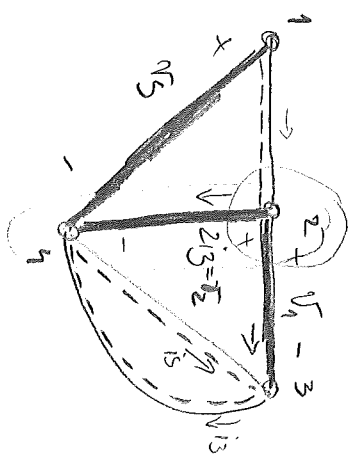

$$v_2 + i_3 R_3 = 2i_3 \Rightarrow v_1 = 2i_3 - i_3 R_3$$

Node ③:

$$\frac{v_1}{R_2} + i_5 = \frac{v_2 - v_4}{R_3}$$

Node ②:

$$\frac{v_5 - v_2}{R_1} = \frac{v_1}{R_2} + i_4$$

=>

$$\frac{v_1}{R_2} + i_5 = \frac{2i_3 - v_1}{R_3}$$

2 eqns

2 unknowns