
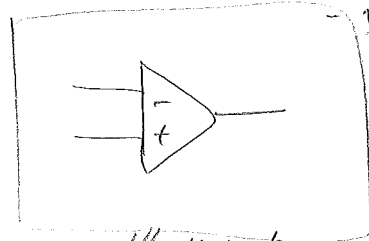



The Operational Amplifier (OpAmp) (OA)

tell about the key techniques
 $\frac{v_o}{v_i}$ always applicable
 $\frac{v_{oc}}{I_{OS}}$ applicable when $v_{oc} \neq 0$
 $i_{sc} \neq 0$.

Symbols:

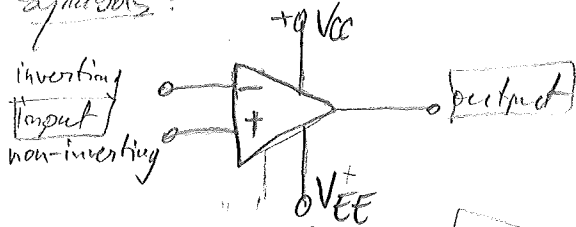

Terminology:

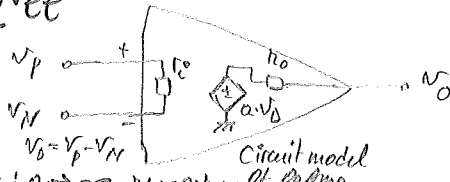


we'll use this

a = unloaded voltage gain; eg: 200,000 V/V
 h_i, h_o = input, output resistances
 v_D = differential input voltage

The ideal OpAmp: $a \rightarrow \infty; h_i \rightarrow \infty; h_o \rightarrow 0$

- no current flows into the inputs!
- there is no voltage difference between the two input terminals
- $h_i \rightarrow \infty, h_o \rightarrow 0, a \rightarrow \infty$

(a) The inverting amplifier

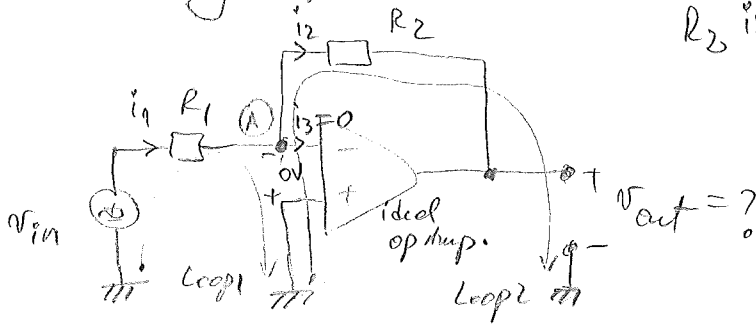

R_2 is the feedback resistor (negative)

KVL:
 Loop 1: $v_{in} - R_1 i_1 + 0 = 0 \Rightarrow i_1 = i_2 = \frac{v_{in}}{R_1}$
 Loop 2: $v_{out} + R_2 i_2 + 0 = 0 \Rightarrow v_{out} + R_2 \cdot \frac{v_{in}}{R_1} = 0$


KCL
 Node ②: $i_1 = i_2 + i_3 = i_2$

$\Rightarrow v_{out} = -\frac{R_2}{R_1} \cdot v_{in}$ (1)

"inverting" amplifier.
 the gain!

- if $R_2 > R_1 \Rightarrow$ gain is an amplification.
- $R_2 < R_1 \Rightarrow$ attenuation.
- $R_1 = R_2 \Rightarrow$ gain is 1; inverted.

(b) Non-inverting amplifier

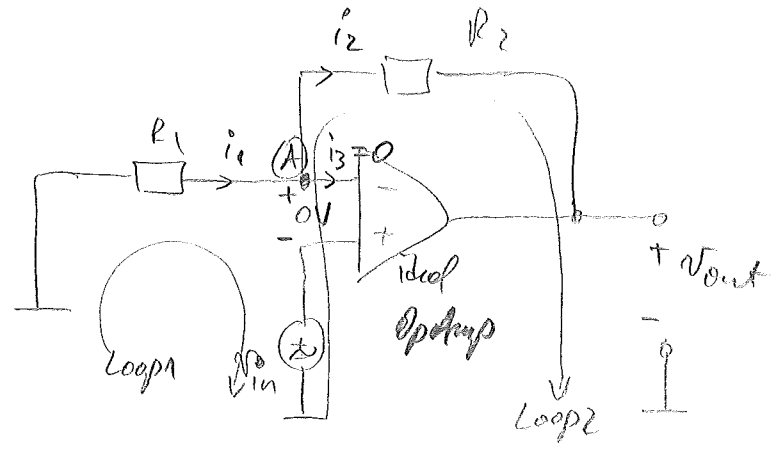


$$\left. \begin{aligned} \text{Loop 1: } & +R_1 i_1 + v_{in} = 0 \\ \text{Loop 2: } & -v_{in} + R_2 i_2 + v_{out} = 0 \\ \text{KCL A: } & i_1 = i_2 - i_3 = i_2 \end{aligned} \right\} \Rightarrow \begin{cases} R_1 i_1 = -v_{in} \Rightarrow i_1 = -\frac{v_{in}}{R_1} \\ -v_{in} + R_2 i_2 + v_{out} = 0 \end{cases}$$

$$-v_{in} - \frac{v_{in}}{R_1} \cdot R_2 + v_{out} = 0$$

$$v_{out} = \left(1 + \frac{R_2}{R_1}\right) v_{in} \quad (2) \quad \text{non-inverting!}$$

Gain: $\frac{v_{out}}{v_{in}} = \left(1 + \frac{R_2}{R_1}\right)$ gain.

(c) Summing amplifier

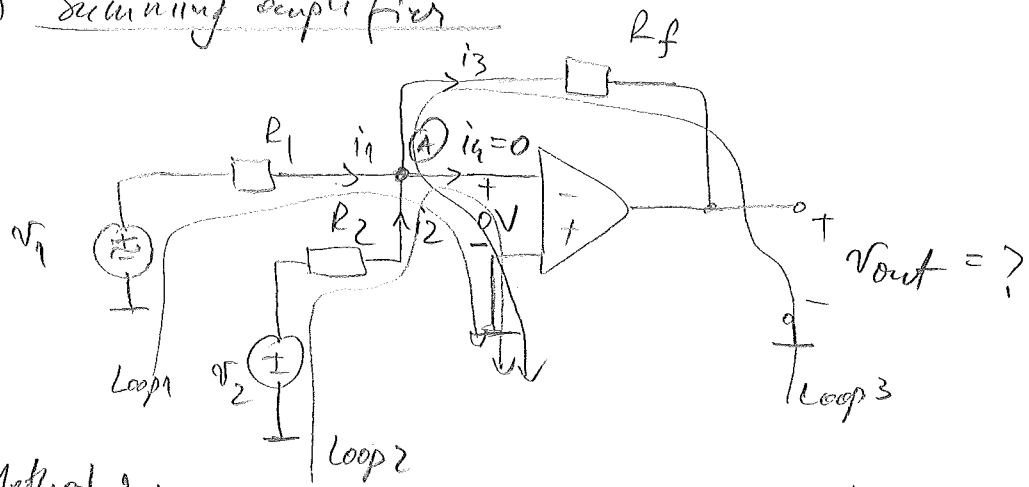

$R_1 = R_2$

Method 1:

$$\text{Loop 1: } v_1 - R_1 i_1 = 0 \Rightarrow i_1 = \frac{v_1}{R_1}$$

$$\text{Loop 2: } v_2 - R_2 i_2 = 0 \Rightarrow i_2 = \frac{v_2}{R_2}$$

KCL $i_1 + i_2 = i_3$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} = -\frac{v_{out}}{R_f}$$

$$\text{Loop 3: } v_{out} + R_f i_3 = 0 \Rightarrow i_3 = -\frac{v_{out}}{R_f}$$

Method 2: use super-position.

$$v_{out} = -\frac{R_f}{R_1} \frac{R_f}{R_2} v_1 - \frac{R_f}{R_2} v_2 \quad (3) \quad \text{See verso}$$