

Ch. 7 Capacitors


• Another passive circuit element. It is a energy storage element.

Reminder: a passive circuit element cannot supply power greater than zero
↳ important over an infinite period of time.

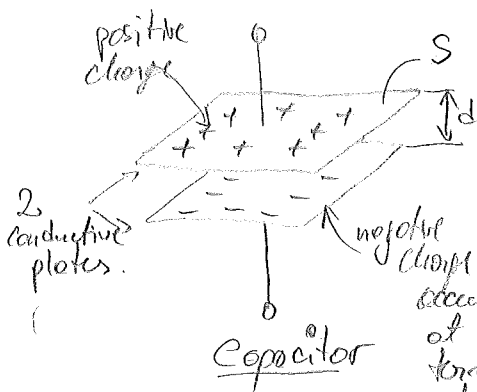(a) **Capacitance** represents the ability of a circuit element to store charge in response to voltage.

Such circuit elements are called **capacitors** or **condensers**

Note: people use capacitance and capacitors interchangeably.



accumulates
of the
terminal
at the lower
potential!



symbol for
capacitance.

The Rate at which the accumulated charge varies with the applied voltage is denoted as capacitance. $C \triangleq \frac{dq_s}{dv}$ (1) [F] Farad is the SI unit

$$1F = \frac{1C}{1V}$$

Capacitance C depends on {
- the area of the plates S
- the distance between plates
- the material ———— ϵ
insulating


$$C = \frac{\epsilon \cdot S}{d} \quad (2)$$

ϵ is permittivity which is $\epsilon_0 = 10^{-9} / (36 \pi)$ F/m for vacuum.

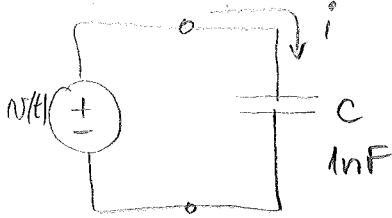
(b) The $i-v$ characteristic

$v \rightarrow q \rightarrow i$

capacitance is increased by $dv \Rightarrow$ charge will increase by $dq = C \cdot dv$ on upper plate and charge will decrease by $dq = C \cdot dv$ on lower plate.



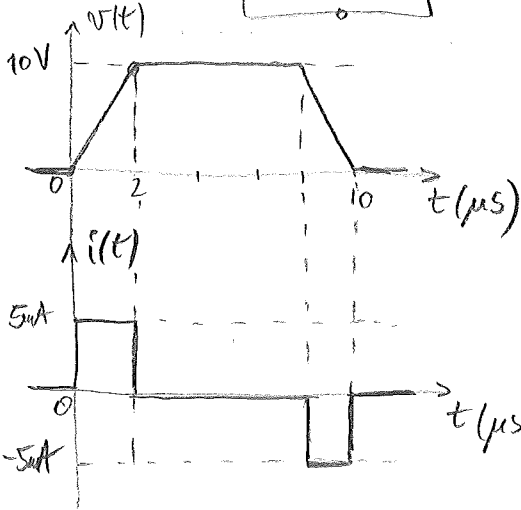indicates \Rightarrow current flows like in the figure! even though no charges actually cross the insulator between plates!



$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

also: $dq = C \cdot dv$



$$i = C \frac{dv}{dt} \quad (2)$$

$$i(t) = C \frac{dv(t)}{dt} \quad (2)$$

The capacitance performs differentiation of voltage!

- Current depends on rate of change of the voltage!
- To sustain current, voltage must change. Otherwise current is zero!
- The more rapidly it changes the larger i !
- One of the most important applications of C : DRAM's.

Example:

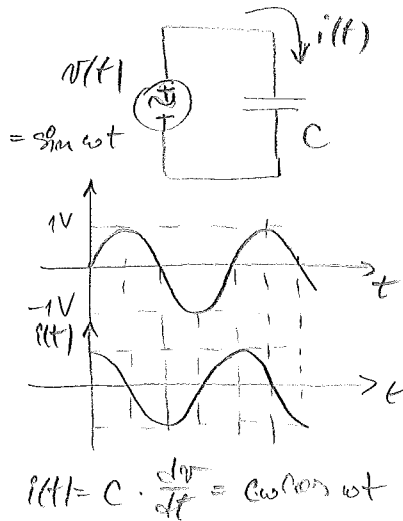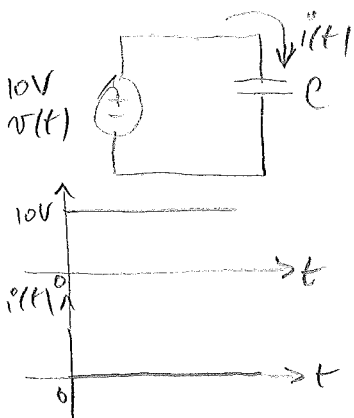

The v-i characteristic

Turn around equation (2): to find the voltage developed by a capacitor in response to an applied varying current.
 pronounced "sai"

$$v(t) = \frac{1}{C} \int_0^t i(\xi) \cdot d\xi + v(0) \quad (3)$$

voltage across the capacitor at time $t=0$.

Seen like this, the capacitor performs the operation of current integration!



$$v(0) = \frac{Q(0)}{C}$$

we deal only with linear capacitances!

$$C = \frac{Q}{V}$$

Particular case: if current is constant: $i(t) = I$
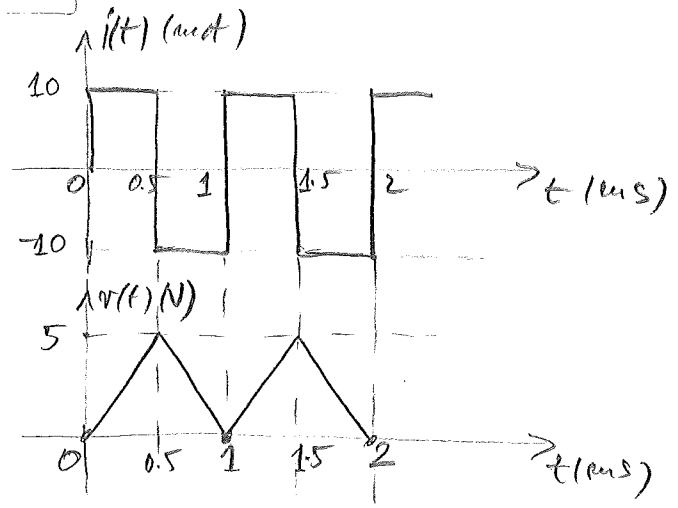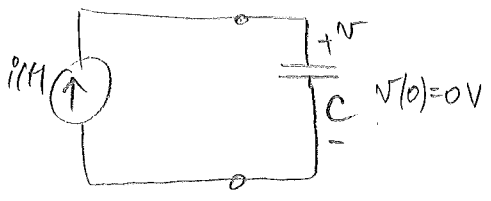
$$\Rightarrow v(t) = \frac{I}{C} \cdot t + v(0) \quad (3')$$



Capacitance Energy

The process of charging a capacitor requires energy expenditure.

Remember: $p = \frac{dW}{dt}$

$$\Rightarrow w(t) = \int_0^t p(\xi) d\xi = \int_0^t v \cdot C \cdot \left(\frac{dv}{d\xi} \right) \cdot d\xi = \int_0^t C v dv = \int_0^t C u du \quad (4)$$

$= v \cdot i = v \cdot C \cdot \frac{dv}{d\xi}$ $= v(\xi) \cdot d\xi = du$ $u = v(\xi)$

variable change (see primo formula da sostituzione di variabile) $v(t)$ (verine spote)

Linear capacitance is for which Q linearly proportional to V .
 $Q = CV$, therefore

$C = \frac{Q}{V}$; we get $w(t) = C \int v dv = C \frac{v^2}{2} \Big|_0^t = C \frac{v(t)^2}{2} = w(t)$ (4)

constant, doesn't depend on v

this is what we'll consider most of the time!

(see verso)

Example

$$C = 1 \mu\text{F}$$

$$V = 10\text{V}$$

$$W = 0.5 \cdot 10^{-6} \times 10^2 = 50 \mu\text{J}$$

Capacitive energy is stored in the form of potential energy in the electric field between plates.

Reminders

① Formula de schimbarea de variabile:

$$\text{fie } \varphi: [a, b] \rightarrow J ; f: J \rightarrow \mathbb{R} ; J \subset \mathbb{R}$$

$\varphi(t)$

(a) f is continuous on J

(b) φ is derivabilă (admits derivative) and its derivative este continuă și diferentiabilă!

$$\int_a^b f(\varphi(t)) \cdot \varphi'(t) dt = \int_{\varphi(a)}^{\varphi(b)} f(x) dx \quad [1]$$

② fie $\varphi: [a, b] \rightarrow [c, d]$; $f: [c, d] \rightarrow \mathbb{R}$

(a) f is continuous pe $[c, d]$

(b) φ is bijectivă, φ, φ^{-1} derivabile și derivabile continue

$$\int_a^b f(\varphi(t)) dt = \int_{\varphi(a)}^{\varphi(b)} f(x) \cdot (\varphi^{-1})'(x) dx \quad [2]$$